

3-Bit Pipeline ADC



Design Project

Dominik Brandstetter (k12110413), Michael Köfinger (k01612781)

336.001 Advanced Integrated Circuit Design SS25

2025-06-02

Overview

- Introduction
- Specifications
- Principle of Operation
- System-Level Simulation
- Digital Core
- ADC Macro Model
- MDAC Design
- Circuit-Level Simulation

Introduction

- Tools
 - IIC_OSIC_TOOLS Docker container
 - IHP SG13G2 open-source PDK
 - Xschem/ngspice/verilator (analog/mixed-signal simulation)
 - Modelsim (digital simulation)
- Objective
 - Design and simulate a 3-bit pipeline ADC w/ 1.5 bit architecture
 - Mixed-signal/level simulation w/ Xschem/ngspice/verilator
 - Digital core using RTL and gate-level simulation
 - Design CMOS OTA
 - ADC: macro models
 - Switches: ideal

Specifications

- $n = 3$ bit
- $n_{1,2} = 1.5$ bit
- $n_3 = 1$ bit
- $f_s = 2$ MHz
- $V_{DD} = 1.5$ V
- $V_{ref} = V_{DD}$

Principle of Operation

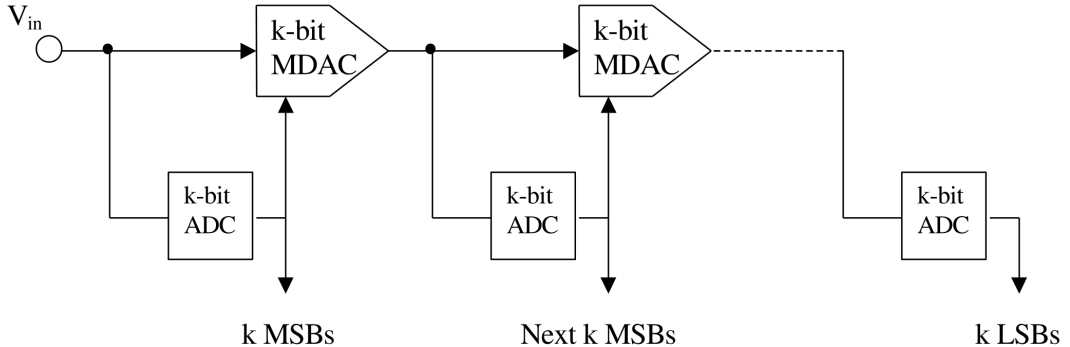


Figure 1: Block diagram.

System-Level Simulation

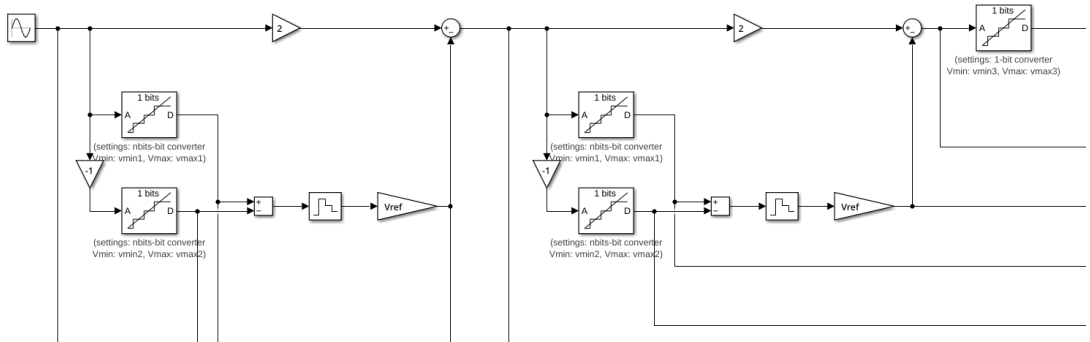


Figure 2: Simulink model.

System-Level Simulation cont'

 


Figure 3: $A_{\text{sig}} = 1 \text{ V}_{\text{peak}}$ $f_{\text{sig}} = 1 \text{ kHz}$

3-bit Implementation w/ 1.5-bit Architecture

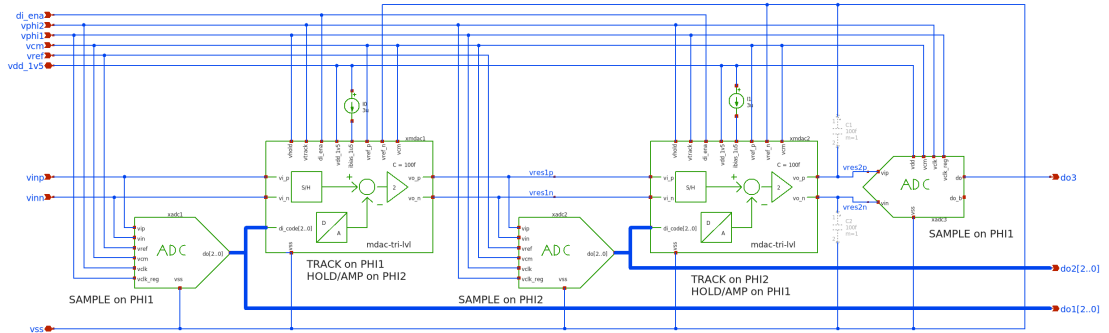


Figure 4: Schematic of ADC core.

Digital Core

- Add ADC outputs from each stage
- RTL simulation using Modelsim and Xschem
- Digital models generated from Ngspice circuits
- HDL (Verilog) used for digital model implementation
- Verilator creates a .so (shared object) file (referenced by Xschem symbol)

 


Figure 5: Summation.

Digital Core cont'

- Modelsim simulation

 


Figure 6: Summation.

Digital Core cont'

- Synthesis using Yosys (generating a xspice-file)
- Target size 100 x 100 μm

 


Figure 7: Layout after P&R.

Tri-Level ADC Macro Model

- Ideal comparator implemented using ADC bridges
- Data is latched during vclk and synchronized on the rising edge of vclk_reg
- Use DAC bridges to convert analog signals to digital format

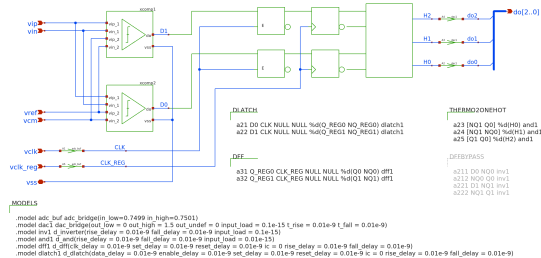


Figure 8: ADC macro model.

MDAC Design

- Sample/Track and hold, k-bit DAC, subtract and amplify

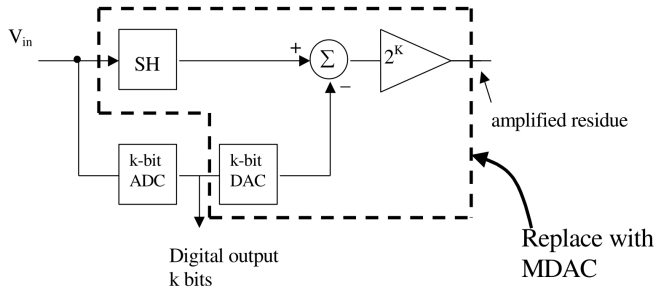


Figure 9: MDAC block diagram.

MDAC Design cont'

- $V_{\text{out}}[n+1] = -2V_{\text{in}}[n] - V_{\text{ref}}[n+1]$

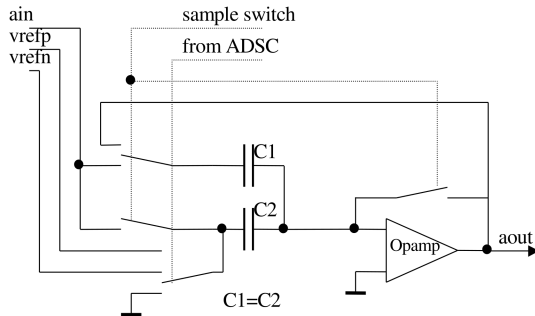


Figure 10: MDAC schematic (single-ended).

MDAC Design cont'

- Fully-differential: invert input to get desired operation

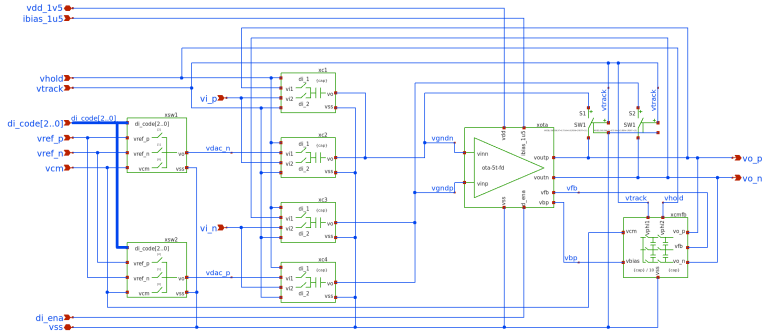


Figure 11: MDAC schematic (fully-differential).

MDAC Design cont'

- $V_o(t) = -V_{\text{step}} \frac{1}{\beta} \frac{L_0}{1+L_0} (1 - e^{-t/\tau_o}) \rightarrow \epsilon_d = e^{-t/\tau_o}$
- $\tau_o \approx \omega_{\text{ug}}$
- Settling accuracy: $\epsilon_{d,\text{target}} = 1/2^{n-n_1} = 2^{-2} = 0.25$
- $T_{\text{settle}} = 1/f_s/2$
- $N_{\text{settling}} = \frac{T_{\text{settle}}}{\tau_o} = -\ln(\epsilon_{d,\text{target}}) = 1.4 \rightarrow 2$
- $C_1 = C_2 = 100 \text{ fF}$ (sufficient in terms of kT/C noise for 3-bit)
- DC gain from static error
- Slew-rate: $\text{SR} = V_{o,\text{step}}/T_{\text{settle}} = I_d/C_{\text{load}}$
- \rightarrow use gm/Id design script for OTA design

MDAC Design cont'

- Keep it simple: basic 5T OTA w/ SC-CMFB (account for additional loading)

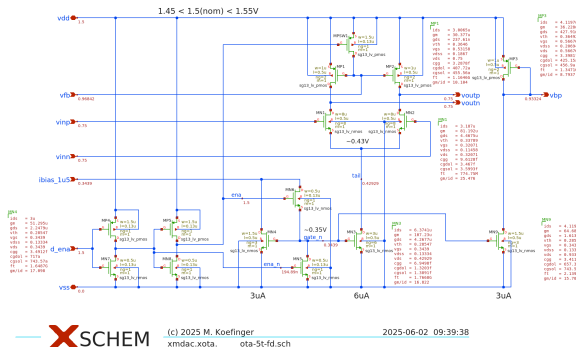


Figure 12: 5T-OTA schematic (ac-params annotated)

Circuit Level Simulation

 
 


Figure 13: $A_{\text{sig}} = 1 \text{ V}_{\text{peak}}$ $f_{\text{sig}} = 1 \text{ kHz}$

Circuit Level Simulation

 
 


Figure 14: 100 Hz triangle input and scaled code; code only

Summary and Known Issues

- Gain error
- ADC macro only handles $f_{\text{sig}} < f_{\text{s}}/10$
- Redesign OTA for more gain (different architecture e.g. two-stage, folded-cascode)
- INL, DNL calculation is missing